Exercice 2

2)
$$Z_0 = \frac{Uelf}{I_0} = R + r = > R = \frac{Uelf}{I_0} - r$$

AN $R = \frac{5}{1,910^2} - 5 = 258,150$

$$=) L = \frac{1}{4\pi^2 \varphi^2 A f^2 C} = \frac{1}{4 \times 10 \times 49 \times (15)^2 \cdot 310^6}$$

$$= 0.175 H$$

4)
$$Z = \frac{\text{Uess}}{\text{Iest}} = \frac{\text{Uess}}{\text{I}} = \sqrt{2} \cdot \frac{\text{Uests}}{\text{Io}}$$

$$= \sqrt{2}! \cdot Z_o = (R+r) \sqrt{2} = 372,15 \Omega$$

Exercice 3

1) le phénomère de la résonance

2)
$$Z_0 = R + r = \frac{UeM}{I_0} = \frac{30}{63,910^3}$$

 $r = \frac{30}{63,910^3} - R = \frac{30}{63,910^3} - 460$
 $= 9,48\Omega$

3)
$$L = \frac{1}{4\pi^2 N_0^2 C} = \frac{1}{4 \times 10 \times (470)^2 \times 5.10^6}$$

= 0,0226H
= 226mH

